 


---

---

# Low Power Design in CMOS




# Why worry about power?

## -- Heat Dissipation



### microprocessor power dissipation

source : arpa-esto

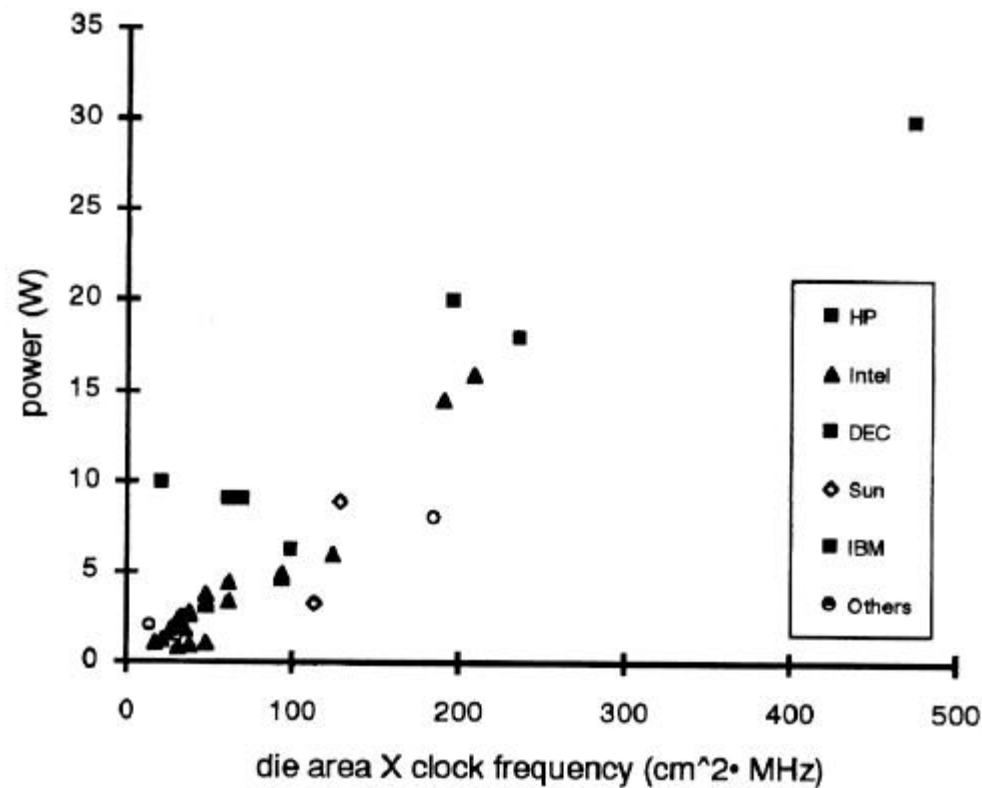


DEC 21164


# Evolution in Power Dissipation

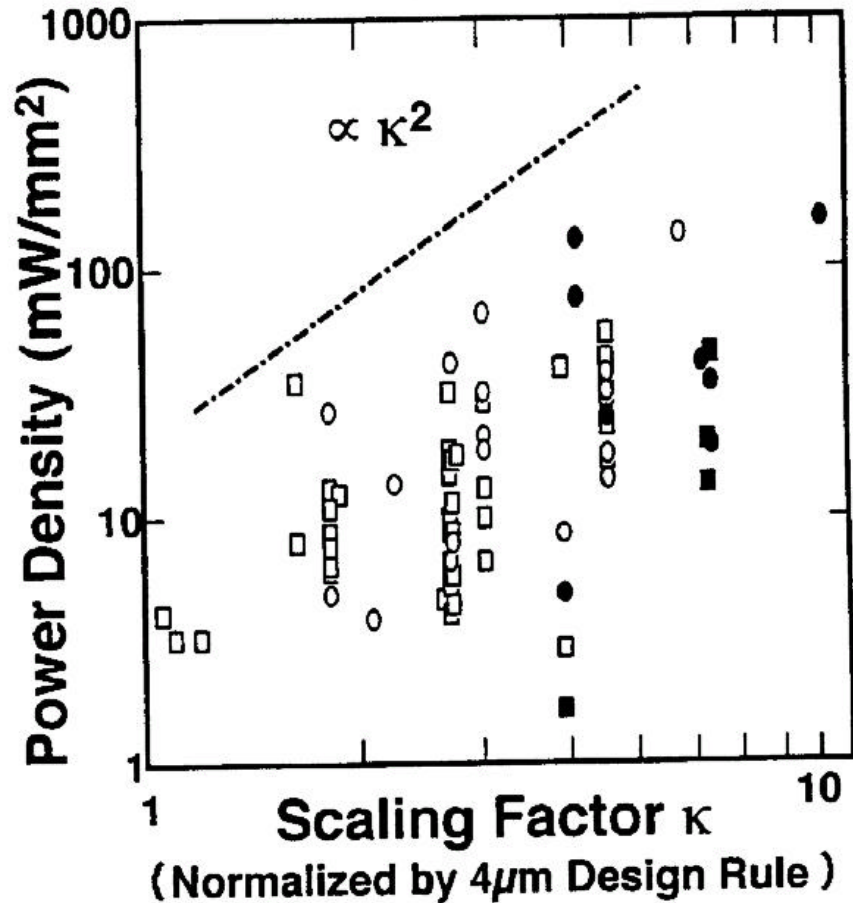 

# Why worry about power – Portability

 

 **Multimedia Terminals**  
**Laptop Computers**  
**Digital Cellular Telephony**



**Expected Battery Lifetime increase  
over next 5 years: 30-40%**

# Where Does Power Go in CMOS?

---

- **Dynamic Power Consumption**

Charging and Discharging Capacitors


- **Short Circuit Currents**

Short Circuit Path between Supply Rails during Switching

- **Leakage**

Leaking diodes and transistors

# Dynamic Power Consumption

 

$$\text{Energy/transition} = C_L * V_{dd}^2$$

$$\text{Power} = \text{Energy/transition} * f = C_L * V_{dd}^2 * f$$

- Not a function of transistor sizes!
- Need to reduce  $C_L$ ,  $V_{dd}$ , and  $f$  to reduce power.

# Dynamic Power Consumption - Revisited

---

**Power = Energy/transition \* transition rate**

$$= C_L * V_{dd}^2 * f_{0 \rightarrow 1}$$

$$= C_L * V_{dd}^2 * P_{0 \rightarrow 1} * f$$

$$= C_{EFF} * V_{dd}^2 * f$$

**Power Dissipation is Data Dependent**  
**Function of *Switching Activity***

$$C_{EFF} = \text{Effective Capacitance} = C_L * P_{0 \rightarrow 1}$$

# Power Consumption is Data Dependent

## Example: Static 2 Input NOR Gate

A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0

Truth Table of 2 input NOR gate

Assume:

$$P(A=1) = 1/2$$

$$P(B=1) = 1/2$$

Then:

$$P(\text{Out}=1) = 1/4$$

$$\begin{aligned} P(0 \rightarrow 1) &= P(\text{Out}=0).P(\text{Out}=1) \\ &= 3/4 \times 1/4 = 3/16 \end{aligned}$$

$$C_{\text{EFF}} = 3/16 * C_L$$



# Transition Probabilities for Basic Gates


---

	$P_{0 \rightarrow 1}$
<b>AND</b>	$(1 - P_A P_B) P_A P_B$
<b>OR</b>	$(1 - P_A)(1 - P_B)(1 - (1 - P_A)(1 - P_B))$
<b>EXOR</b>	$(1 - (P_A + P_B - 2P_A P_B))(P_A + P_B - 2P_A P_B)$

Switching Activity for Static CMOS

$$P_{0 \rightarrow 1} = P_0 \cdot P_1$$
 
# Transition Probability of 2-input NOR Gate




$$p_1 = (1-p_a) (1-p_b)$$

$$p_{0 \rightarrow 1} = p_0 p_1 = (1-(1-p_a) (1-p_b)) (1-p_a) (1-p_b)$$

- $\alpha_{0 \rightarrow 1}$  is a strong function of signal statistics


# Problem: Reconvergent Fanout

 

$$P(Z=1) = P(B=1) \cdot P(X=1 \mid B=1)$$

**Becomes complex and intractable real fast**

# How about Dynamic Circuits?

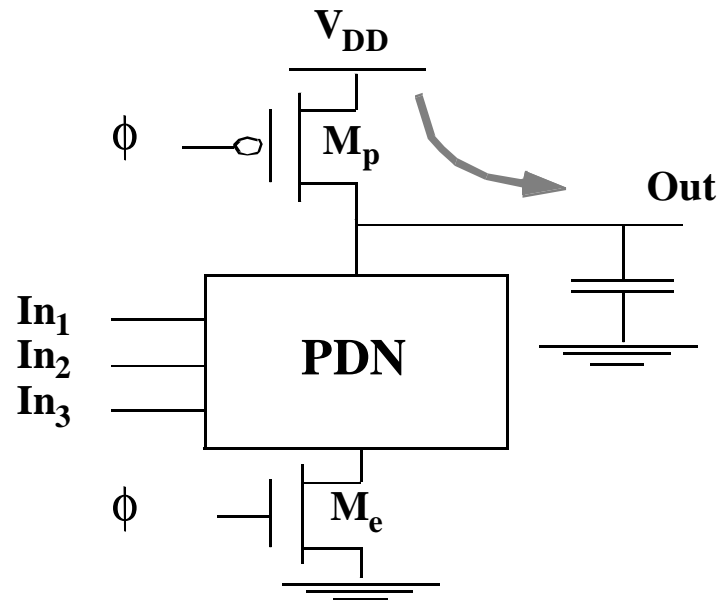

**Power is Only Dissipated when Out=0!**

$$C_{EFF} = P(Out=0).C_L$$

# 4-input NAND Gate

---

## Example: Dynamic 2 Input NOR Gate

A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0

Truth Table of 2 input NOR gate

Assume:

$$P(A=1) = 1/2$$

$$P(B=1) = 1/2$$

Then:

$$P(\text{Out}=0) = 3/4$$

$$C_{\text{EFF}} = 3/4 * C_L$$

**Switching Activity Is Always Higher in Dynamic Circuits**

# Transition Probabilities for Dynamic Gates

---



	$P_{0 \rightarrow 1}$
<b>AND</b>	$(1 - P_A P_B)$
<b>OR</b>	$(1 - P_A)(1 - P_B)$
<b>EXOR</b>	$(1 - (P_A + P_B - 2P_A P_B))$

Switching Activity for Precharged Dynamic Gates

$$P_{0 \rightarrow 1} = P_0$$



# Glitching in Static CMOS

also called: dynamic hazards

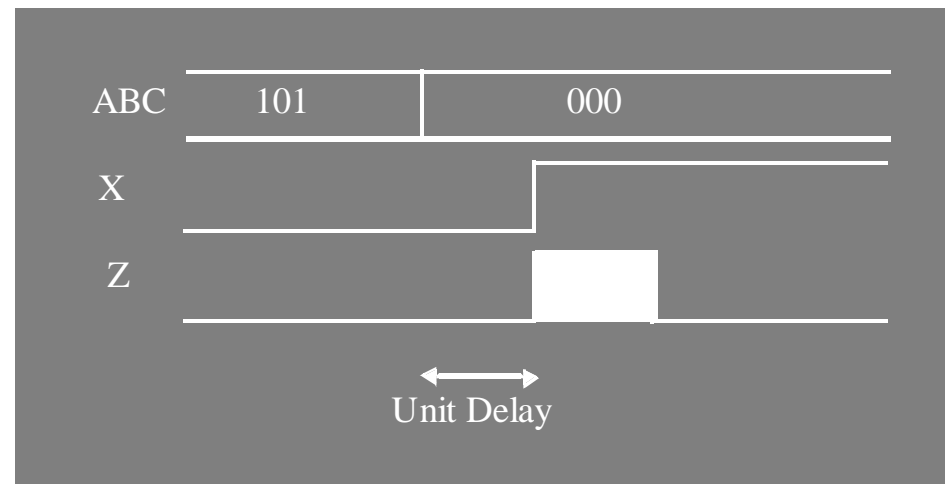 



Observe: No glitching in dynamic circuits

# Example 1: Chain of NOR Gates

  




# Example 2: Adder Circuit

  



# How to Cope with Glitching?

---

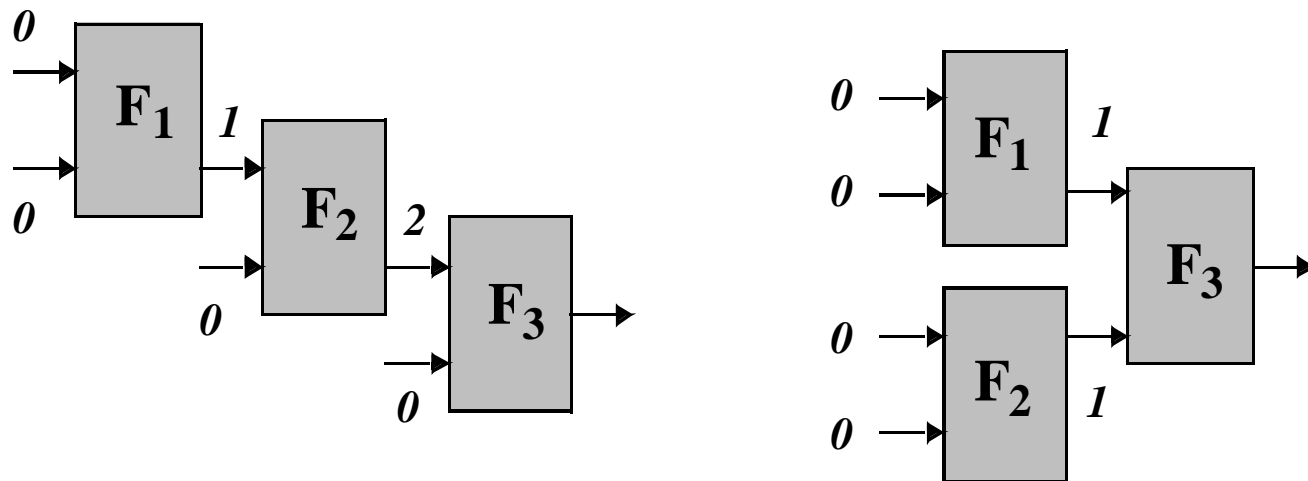


**Equalize Lengths of Timing Paths Through Design**


# Short Circuit Currents

 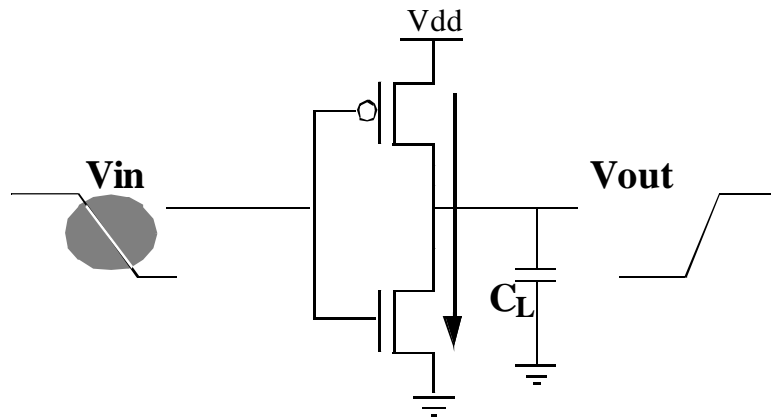
 
# Impact of rise/fall times on short-circuit currents




Large capacitive load

 

Small capacitive load

 
# Short-circuit energy as a function of slope ratio



**The power dissipation due to short circuit currents is minimized by matching the rise/fall times of the input and output signals.**

# Static Power Consumption


---

 

$$P_{stat} = P_{(I_n=1)} \cdot V_{dd} \cdot I_{stat}$$


- Dominates over dynamic consumption
- Not a function of switching frequency

# Leakage

 

**Sub-Threshold Current Dominant Factor**


# Sub-Threshold in MOS

 

**Lower Bound on Threshold to Prevent Leakage**



# Power Analysis in SPICE

 


**Equivalent Circuit for Measuring Power in SPICE**

$$C \frac{dP_{av}}{dt} = k i_{DD}$$

or


$$P_{av} = \frac{k}{C} \int_0^T i_{DD} dt$$

# Design for Worst Case

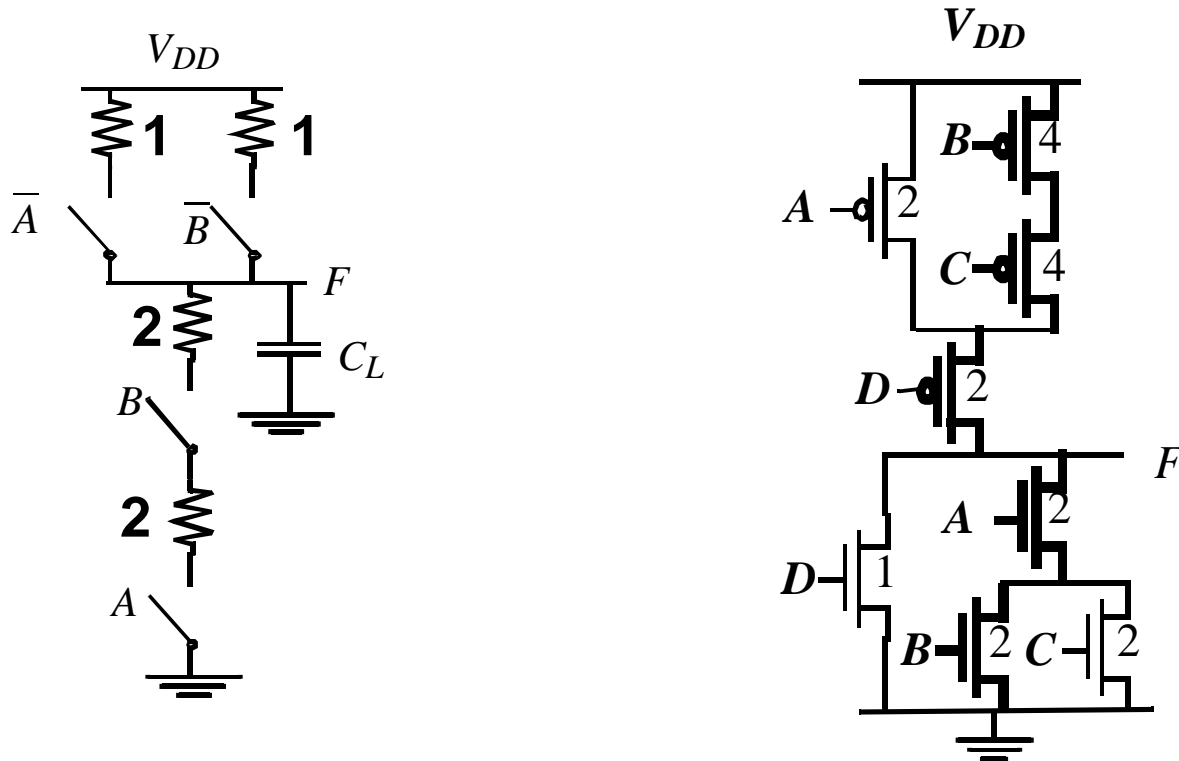

Here it is assumed that  $R_p = R_n$

# Reducing $V_{dd}$

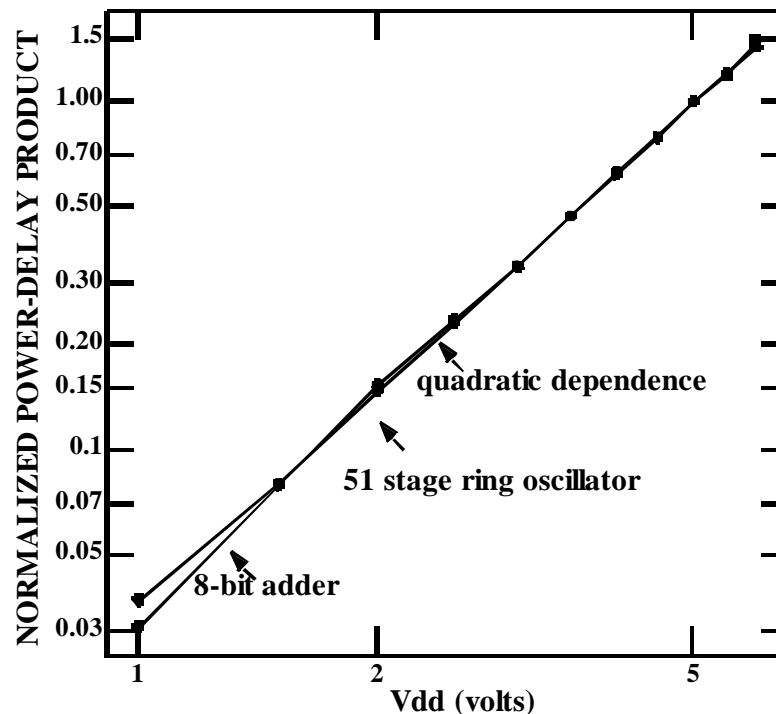


$$P \times t_d = E_t = C_L * V_{dd}^2$$

$$\frac{E(V_{dd}=2)}{E(V_{dd}=5)} = \frac{(C_L) * (2)^2}{(C_L) * (5)^2}$$

$$E(V_{dd}=2) \approx 0.16 E(V_{dd}=5)$$

- Strong function of voltage ( $V^2$  dependence).
- Relatively independent of logic function and style.
- Power Delay Product Improves with lowering  $V_{DD}$ .

# Lower $V_{dd}$ Increases Delay

 


$$T_d = \frac{C_L * V_{dd}}{I}$$

$$I \sim (V_{dd} - V_t)^2$$

$$\frac{T_d(V_{dd}=2)}{T_d(V_{dd}=5)} = \frac{(2) * (5 - 0.7)^2}{(5) * (2 - 0.7)^2} \approx 4$$

- Relatively independent of logic function and style.

# Lowering the Threshold

 

**Reduces the Speed Loss, But Increases Leakage**

**Interesting Design Approach:**  
**DESIGN FOR  $P_{\text{Leakage}} == P_{\text{Dynamic}}$**


# Transistor Sizing for Power Minimization

---

Lower Capacitance

Higher Voltage

Small W/L's

 


Large W/L's

Higher Capacitance

Lower Voltage

- Larger sized devices are useful only when interconnect dominated.
- Minimum sized devices are usually optimal for low-power.

# Transistor Sizing for Fixed Throughput

 

$C_{\text{MIN}}$  = Minimum sized gate ( $W/L=1$ )

$W/L$  after sizing

$$\alpha = C_P / (K C_{\text{MIN}})$$

## HIGH PERFORMANCE


$$W/L \gg C_P / (K C_{\text{MIN}})$$

## LOW POWER

$$W/L = 2 C_P / (K C_{\text{MIN}})$$


(if  $C_P \geq K C_{\text{MIN}}$ )

$$\text{ELSE } W/L = 1$$

 


# Reducing Effective Capacitance

---

 

Global bus architecture

 

Local bus architecture

**Shared Resources incur Switching Overhead**



# Summary

---

- **Power Dissipation is becoming Prime Design Constraint**
- **Low Power Design requires Optimization at all Levels**
- **Sources of Power Dissipation are well characterized**
- **Low Power Design requires operation at lowest possible voltage and clock speed**

